

Different chapter = red mark

Out of syllabus = blue mark

Chapter 3: Boolean Algebra and Simplification

- 2019-20 Midterm: Simplify the Boolean function $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ with don't-care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$ and show "An expression with the minimum number of literals is not necessarily unique."
- 2020-21 Midterm: Simplify the Boolean function $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ with don't-care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$ and show that an expression with the minimum number of literals is not necessarily unique.
- 2020-2021 Final: Simplify $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ with don't care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$ and show that an expression with the minimum number of literals is not necessarily unique.
- 2020-2021 Final: Find the complement of the function $F(x, y, z) = x(y' + z')z$ and $F(x, y, z) = yz + y'z$ using De Morgan's theorem.
- 2020-2021 Final: Prove that $\Sigma m(0, 1, 2, 3, 4, 5, 6, 7) = \Pi M(8, 9, 10, 11, 12, 13, 14, 15)$.
- 2020-2021 Final: Consider $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$. Find out and show prime implicants and essential prime implicants by the Karnaugh map from the above expression.
- 2020-2021 Final: Simplify the following Boolean function by using the tabulation method: $F = \Sigma(0, 1, 2, 8, 10, 11, 14, 15)$.

Chapter 4: Combinational Logic

- 2019-20 Midterm: What are the purposes of arithmetic circuits? Design and describe a 4-bit full adder with a look-ahead carry generator.
- 2020-2021 Final: Implement the following Boolean function using only NAND gates (a universal gate): $F(A, B, C, D) = A'B'C'D + ABC'D' + A'B'CD$.
- 2020-2021 Final: Realize with all NOR gates a NAND gate.
- 2020-2021 Final: Implement the following Boolean function in multilevel NAND gates: $F = A(B + CD) + BC$
- 2019-20 Midterm: Design a logic circuit to determine a prime number ranging from 0 to 15.

Decimal A B C D Y (Prime?)

0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1

Decimal A B C D Y (Prime?)

8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

- 2020-21 Midterm: Why is code conversion needed? Design a BCD to Excess-3 converter with Boolean functions, a logic diagram, a truth table, and a proper description.
- 2020-2021 Final: A four-bit binary number is represented as A₃A₂A₁A₀, where A₃, A₂, A₁, and A₀ represent the individual bits and A₀ is equal to the LSB. Design a logic circuit that will produce a HIGH output whenever the binary number is greater than 0010 and less than 1000.

Decimal A₃ A₂ A₁ A₀ Y (Output)

0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0

- 2020-2021 Final: Define universal gate. Implement a combinational circuit which converts a four-bit excess-3 code to a four-bit BCD code.

বই এ যেটা দেয়া আছে সেটার উল্টো কাহিনী

courtesy :: ওমর ফারুক তানভির + chatGPT